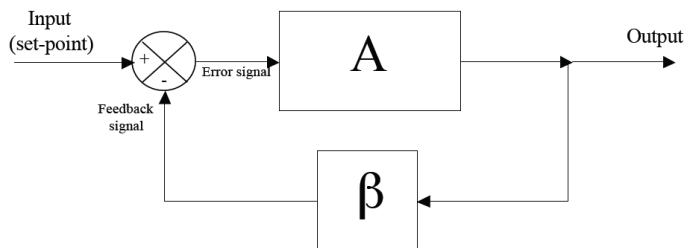


Summary of lecture 2 (28th November 2019)

Control systems, PID control, and Operational amplifiers

Generic negative-feedback control system:



$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta}$$


If the open-loop gain of the system is very high, such that $A\beta \gg 1$ then

the gain simplifies to $\frac{V_{out}}{V_{in}} = \frac{1}{\beta}$ so the


gain depends only on the FEEDBACK term, not the open-loop gain.

PID control:

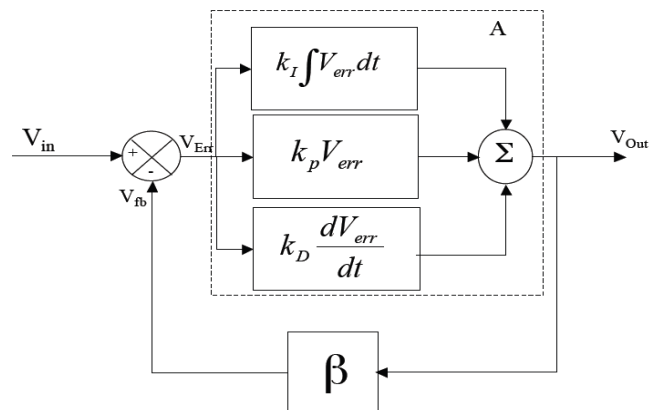The **proportional+differential+integral** (PID) control system is an improvement to the 'bang-bang' (on-off) and proportional control systems.



The 'Operational amplifier' (op-amp):

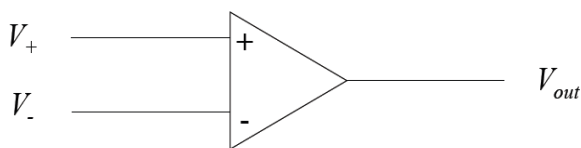

$$V_{out} = A(V_+ - V_-)$$


The open-loop gain (A) of an op-amp is very large, $\sim 10^5 - 10^8$.

Note: Op-amps *also* require dc power connections to operate – these are often not shown on schematic circuit diagrams!


'Golden Rules' for op-amps with negative-feedback:

1. The output drives such that the inputs are at the same voltage
2. No current flows into the inputs
3. Loading does not affect the output

Note: these only apply for negative feedback with $A\beta \gg 1$.

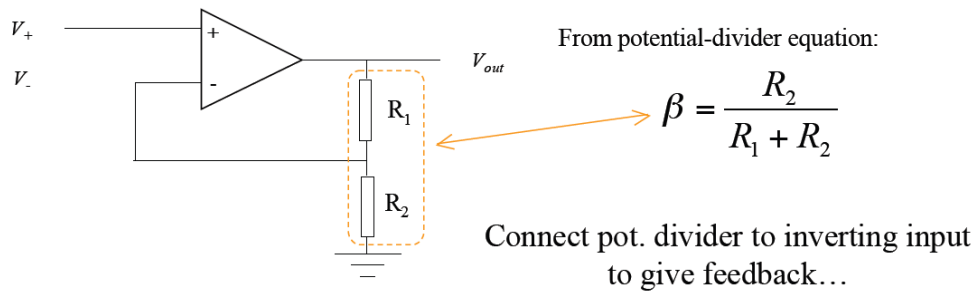Non-inverting amplifier:

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{1}{\beta} = 1 + \frac{R_1}{R_2}$$

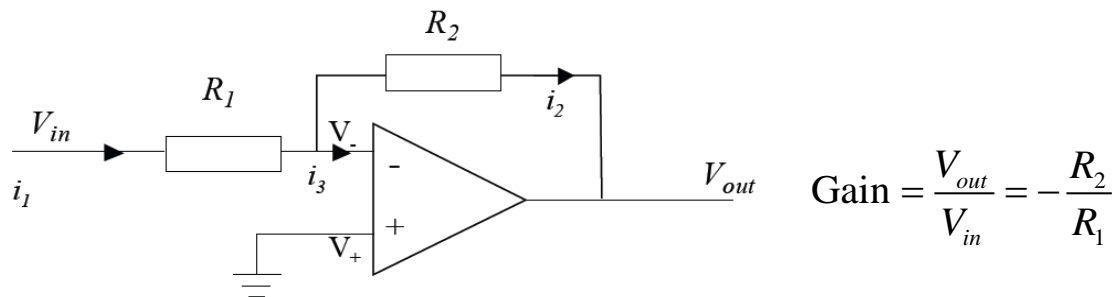Inverting amplifier:**Integrator:**